



# Fast-Transient Low-Dropout Regulator

# Main Points



- Introduction
- Design specs
- Design methodology
- Simulation results
- Design challenges

# Introduction



- **Who are we**
- **Our goals**
  - Robust power management unit
- **What is an LDO**
  - Is it really an LDO?

# Design Specs



Parameter	Name	Min	Typ	Max	Units	Comments
Power Supply Voltage	Vin	2.4		3.5	V	Large range for drop out
Output Voltage	Vout	0.85	1	1.25	V	Programmable with 12.5 mV step
Untrimmed Output Voltage Accuracy			±6		%	
Load Current	Iout	0.1		150	mA	Large range of current
Vin Ramp Rate	dVin/dt			0.2	mV/μs	
Rate of Iout Change	dIout/dt			5	mA/ns	Load transient regulation for maximum load variation at maximum capacitance
Undershoot/Overshoot				50	mV	
Load Capacitance	CL			1	nF	Not a large enough
Power Supply Rejection at 1 MHz	PSR1MHz	30			dB	
Power Supply Rejection at 10 MHz	PSR10MHz	20			dB	
Line Regulation			2		mV/V	
Load Regulation			50		mV/A	


# Design Methodology

- LDO Topology

We want a stable fast-transient topology

- Error Amplifier's Topology

How is the input and output's swings?

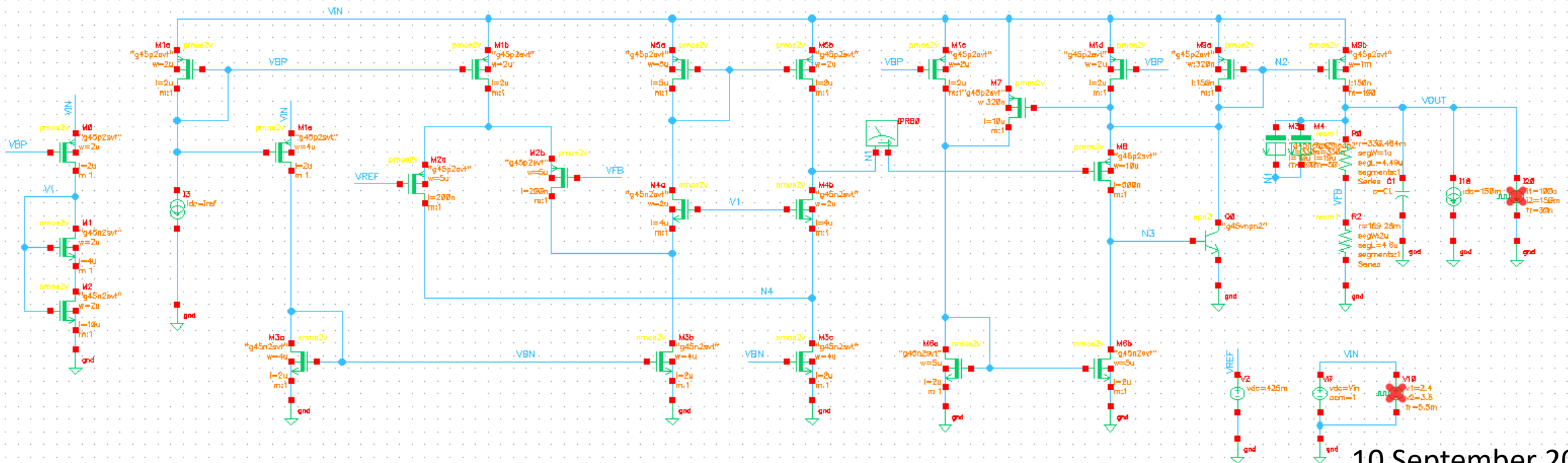

# Design Methodology



- **Static gain error**  
Map it into  $V_{ref}$ ,  $\beta$  and  $A_{v_{error\ amplifier}}$ .
- **Stability constraints**  
Hard to achieve. What about Miller compensation?
- **Load and Line regulation**  
How to make the current change negligible?
- **Achieving PSR proposals**

# Simulation Results



1. DC operating parameters simulation
2. Transient load simulation
3. Transient input simulation
4. Stability analysis and PSR
5. Figure of merit
6. Specs achieved




Evaluated at Minimum *loop gain* (minimum  $V_{in}$  & minimum  $\beta$ )



# Transient Load Simulation


## 1. Load regulation

 

# Transient Load Simulation


1. Load regulation

2. Overshoot

 

# Transient Load Simulation

 
1. Load regulation
2. Overshoot
3. Undershoot



# Transient Input Simulation



## 1. Line regulation

 


10 September 2024

# Stability Analysis and PSR

## 1. Phase Margin

loop gain phase

■ loop gain in dB  
■ loop gain phase

 


10 September 2024

# Stability Analysis and PSR

## 1. Phase Margin

## 2. PSR

 

# Figure of Merit



$$FOM = \frac{C_L * \Delta V_{out} * I_Q}{I_{L,max}^2} = 2.16 * 10^{-6} (ns)$$



# Achieved Specs



Spec	Required	Achieved
Technology used	45nm CMOS	
Supply Voltage	2.4 V $\rightarrow$ 3.5 V	—
Output Voltage	0.85 V $\rightarrow$ 1.25 V	—
Untrimmed output voltage accuracy	$< \pm 6\%$	1%
Load Current	0.1 mA $\rightarrow$ 150 mA	—
Undershoot/Overshoot	$< 50$ mV	27 mV
Phase margin	$> 45^\circ$	49°
Max Load Capacitance	1 nF	—
Line Regulation	$< 2$ mV/V	1.7 mV/V
Load Regulation	$< 50$ mV/A	9 mV/A
Power Supply Rejection at 1 MHz	30 dB	10 dB
Power Supply Rejection at 10 MHz	20 dB	4 dB
FOM	—	$2.16 * 10^{-6}$ (ns)

10 September 2024

# Design Challenges



## 1. PSR

Bypass device length, low-pass filter and El-Nozahy's paper

## 2. Load regulation

Magical mismatch effect

## 3. Line regulation

Decrease the bypass current change

# Thank You

## **Presented by:**

Mohamed Essam

Bilal Ramadan

Abdelrahman Abohendy

Mahmoud Saker