

# Fast-Transient Low-Dropout Regulator

#### **Main Points**



- Introduction
- Design specs
- Design methodology
- Simulation results
- Design challenges

#### Introduction



- 1. Who are we
- Our goalsRobust power management unit
- 1. What is an LDO Is it really an LDO?


# Design Specs


 
# Design Methodology



- LDO Topology
   We want a stable fast-transient topology
- Error Amplifier's Topology
   How is the input and output's swings?



#### Design Methodology



- Static gain error Map it into  $V_{ref}$ ,  $\beta$  and  $A_{v_{error\ amplifier}}$ .
- Stability constraints
   Hard to achieve. What about Miller compensation?
- Load and Line regulation
   How to make the current change negligible?
- Achieving PSR proposals

#### Simulation Results




- 1. DC operating parameters simulation
- 2. Transient load simulation
- 3. Transient input simulation
- 4. Stability analysis and PSR
- 5. Figure of merit
- 6. Specs achieved

#### DC OP Simulation


 
#### 1. Max output error


Evaluated at Minimum  $loop\ gain$  (minimum  $V_{in}$  &minimum  $\beta$ )



## **Transient Load Simulation**



#### 1. Load regulation

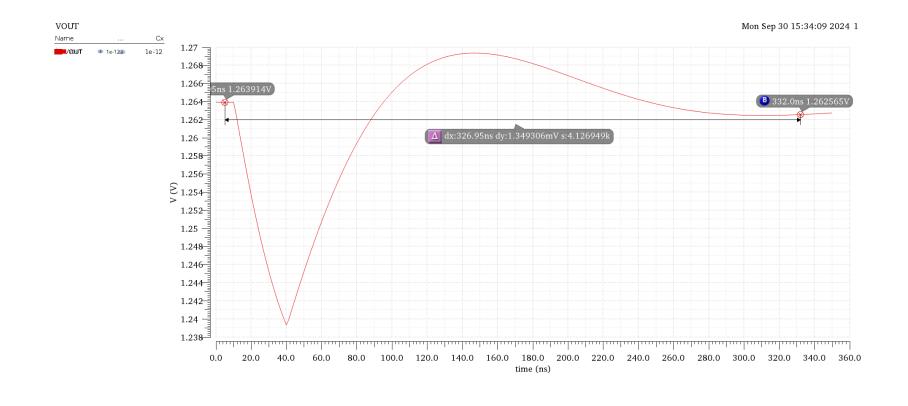


## **Transient Load Simulation**



1. Load regulation


2. Overshoot

 

## **Transient Load Simulation**



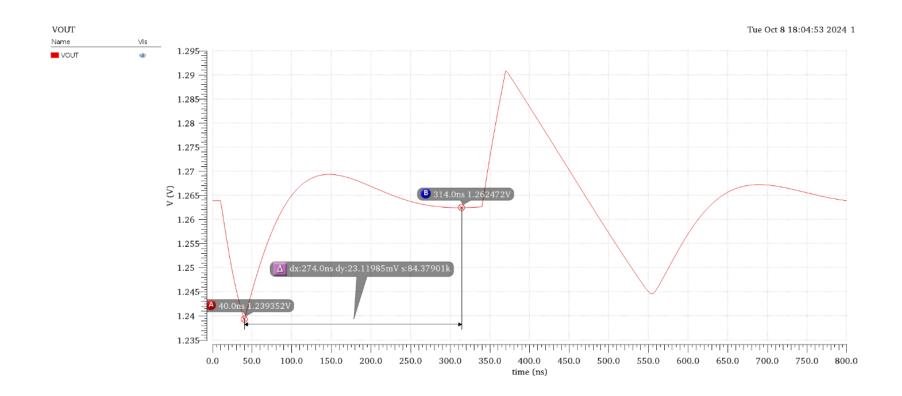
- 1. Load regulation
- 2. Overshoot
- 3. Undershoot



# Transient Input Simulation




#### 1. Line regulation

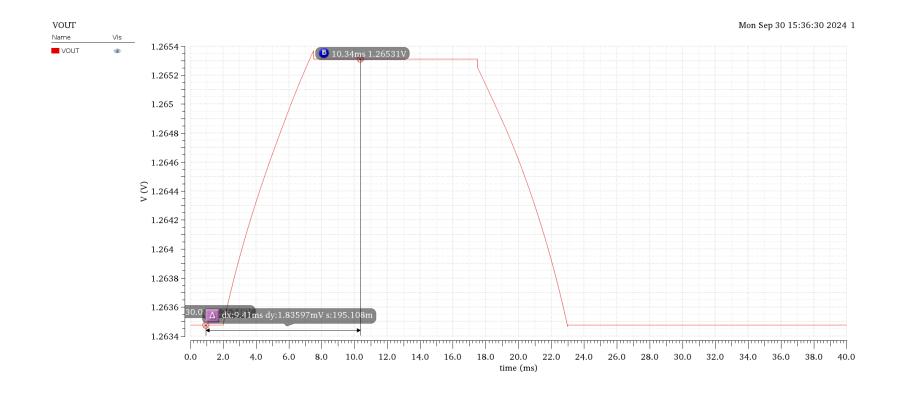

## Stability Analysis and PSR



#### 1. Phase Margin

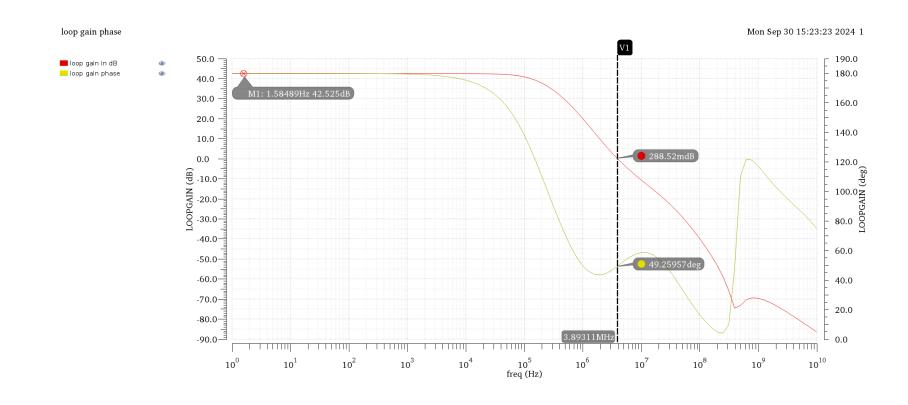


# Stability Analysis and PSR



1. Phase Margin

2. PSR

 

### Figure of Merit



$$FOM = \frac{C_L * \Delta V_{out} * I_Q}{I_{L,max}^2} = 2.16 * 10^{-6} (ns)$$

# **Achieved Specs**



Spec	Required	Achieved
Technology used	45nm CMOS	
Supply Voltage	$2.4~V \rightarrow 3.5~V$	_
Output Voltage	$0.85 V \rightarrow 1.25 V$	-
Untrimmed output voltage accuracy	< ±6%	1%
Load Current	$0.1~mA \rightarrow 150~mA$	-
Undershoot/Overshoot	< 50 mV	27 mV
Phase margin	> 45°	49°
Max Load Capacitance	1 nF	_
Line Regulation	< 2 mV/V	1.7 <i>mV /V</i>
Load Regulation	$< 50 \ mV/A$	9 mV/A
Power Supply Rejection at 1 MHz	30 <i>dB</i>	10 <i>dB</i>
Power Supply Rejection at 10 MHz	20 <i>dB</i>	4 <i>dB</i>
FOM	-	$2.16 * 10^{-6} (ns)$

## Design Challenges



- 1. PSR
  - Bypass device length, low-pass filter and El-Nozahy's paper
- Load regulationMagical mismatch effect
- 3. Line regulation

  Decrease the bypass current change

#### Thank You

Presented by:

**Mohamed Essam** 

Bilal Ramadan

Abdelrahman Abohendy

Mahmoud Saker