



# Fast-Transient Low-Dropout Regulator

# Main Points

- Introduction
- Design specs
- Design methodology
- Simulation results
- Design challenges

# Introduction

1. Who are we
2. Our goals  
Robust power management unit
3. What is an LDO  
Is it really an LDO?

# Design Specs


# Design Methodology

- LDO Topology

## We want a stable fast-transient topology

- Error Amplifier's Topology

## How is the input and output's swings?

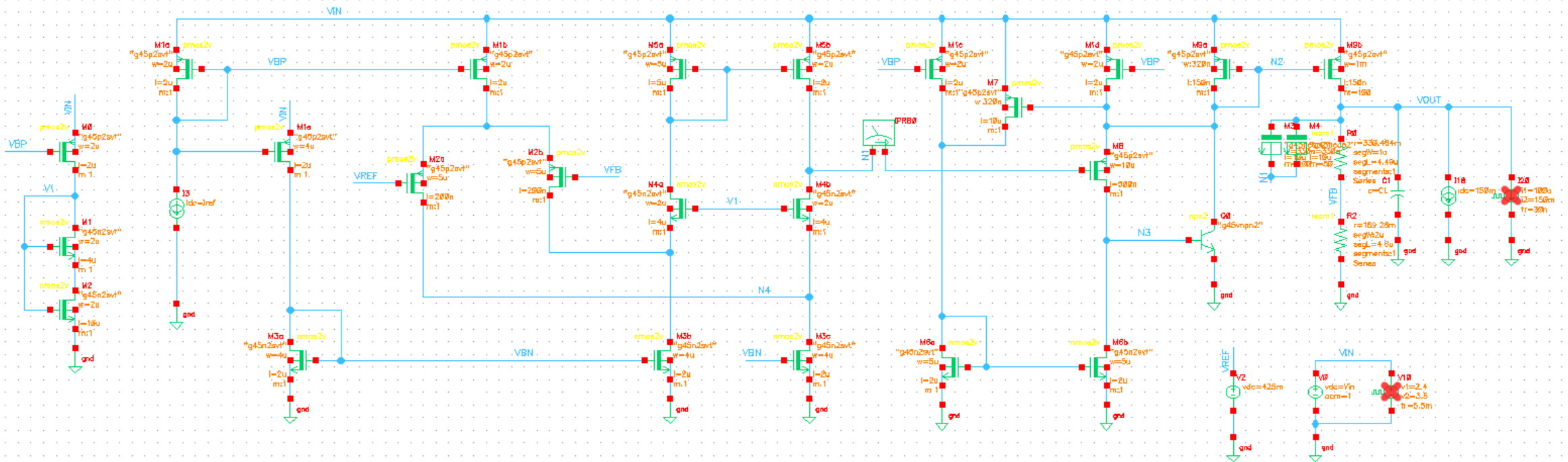

# Design Methodology

- Static gain error

Map it into  $V_{ref}$ ,  $\beta$  and  $A_{v_{error\ amplifier}}$ .

- Stability constraints

Hard to achieve. What about Miller compensation?

- Load and Line regulation

How to make the current change negligible?

- Achieving PSR proposals

# Simulation Results


1. DC operating parameters simulation
2. Transient load simulation
3. Transient input simulation
4. Stability analysis and PSR
5. Figure of merit
6. Specs achieved



# DC OP Simulation

 
## 1. Max output error

Evaluated at Minimum *loop gain* (minimum  $V_{in}$  & minimum  $\beta$ )



# Transient Load Simulation


## 1. Load regulation

 

# Transient Load Simulation


1. Load regulation

2. Overshoot

 


# Transient Load Simulation

 1. Load regulation
2. Overshoot
3. Undershoot




# Transient Load Simulation

## 1. Line regulation

 

# Stability Analysis and PSR


## 1. Phase Margin

 

# Stability Analysis and PSR

## 1. Phase Margin

## 2. PSR

 

# Figure of Merit

$$FOM = \frac{C_L * \Delta V_{out} * I_Q}{I_{L,max}^2} = 2.16 * 10^{-6} (ns)$$



# Achieved Specs

Spec	Required	Achieved
Technology used	45nm CMOS	
Supply Voltage	2.4 V $\rightarrow$ 3.5 V	—
Output Voltage	0.85 V $\rightarrow$ 1.25 V	—
Untrimmed output voltage accuracy	$< \pm 6\%$	1%
Load Current	0.1 mA $\rightarrow$ 150 mA	—
Undershoot/Overshoot	$< 50\text{ mV}$	27 mV
Phase margin	$> 45^\circ$	49°
Max Load Capacitance	1 nF	—
Line Regulation	$< 2\text{ mV/V}$	1.7 mV/V
Load Regulation	$< 50\text{ mV/A}$	9 mV/A
Power Supply Rejection at 1 MHz	30 dB	10 dB
Power Supply Rejection at 10 MHz	20 dB	4 dB
FOM	—	$2.16 * 10^{-6}\text{ (ns)}$

# Design Challenges

1. PSR  
Bypass device length, low-pass filter and El-Nozahy's paper
2. Load regulation  
Magical mismatch effect
3. Line regulation  
Decrease the bypass current change

# Thank You

Presented by:

Mohamed Essam

Bilal Ramadan

Abdelrahman Abohendy

Mahmoud Saker