



Fast-Transient Low-Dropout Regulator

Main Points

Introduction

Design specs

Design
methodology

Simulation
results

FOM and
specs
achieved

Design
challenges

9 October 2024

Introduction



- **Who are we?**
- **Our goals**
 - Robust power management unit
- **What is an LDO?**
 - Is it really an LDO?

9 October 2024

Design Specs

Parameter	Name	Min	Typ	Max	Units	Comments
Power Supply Voltage	Vin	2.4		3.5	V	Large range for drop out
Output Voltage	Vout	0.85	1	1.25	V	Programmable with 12.5 mV step
Untrimmed Output Voltage Accuracy			±6		%	
Load Current	Iout	0.1		150	mA	Large range of current
Vin Ramp Rate	dVin/dt			0.2	mV/μs	
Rate of Iout Change	dIout/dt			5	mA/ns	Load transient regulation for maximum load variation at maximum capacitance
Undershoot/Overshoot				50	mV	
Load Capacitance	CL			1	nF	Not a large enough
Power Supply Rejection at 1 MHz	PSR1MHz	30			dB	
Power Supply Rejection at 10 MHz	PSR10MHz	20			dB	
Line Regulation			2		mV/V	
Load Regulation			50		mV/A	


Design Methodology

- **LDO Topology**

We want a stable fast-transient topology

- **Error Amplifier's Topology**

How is the input and output's swings?

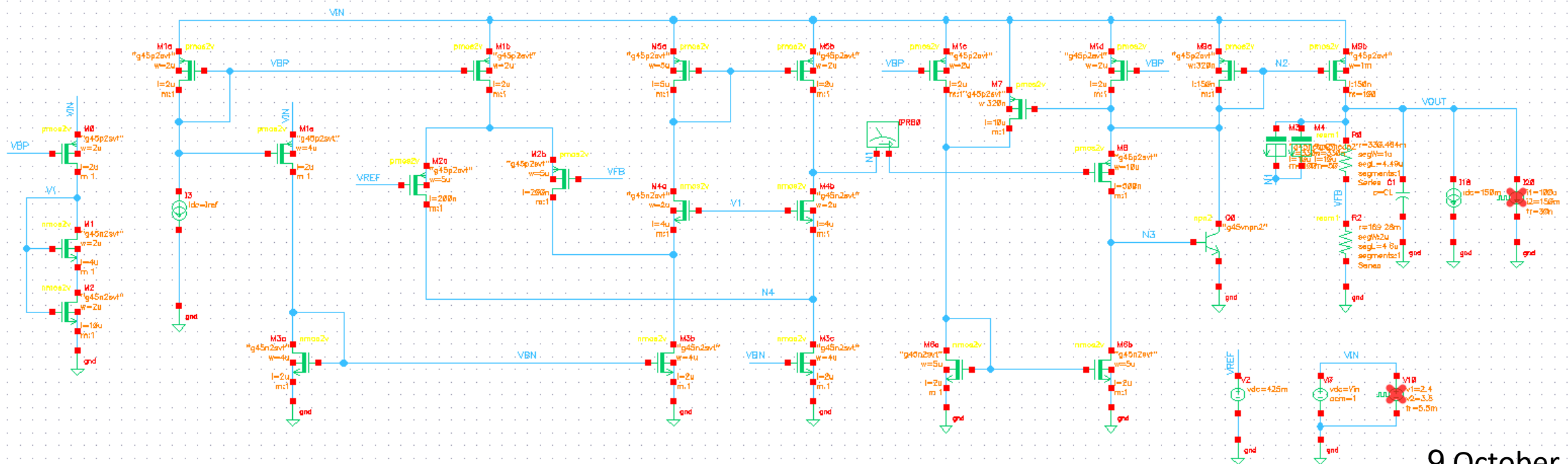

9 October 2024

Design Methodology



- **Static gain error**
Map it into V_{ref} , β and $A_{v_{error\ amplifier}}$
- **Stability constraints**
Hard to achieve. What about Miller compensation?
- **Load and Line regulation**
How to make the current change negligible?
- **Achieving PSR proposals**

Simulation Results




1. DC operating parameters simulation
2. Transient load simulation
3. Transient input simulation
4. Stability analysis and PSR

9 October 2024

DC OP Simulation

 1. Max output error


Evaluated at Minimum *loop gain* (minimum V_{in} & minimum β)



9 October 2024

Transient Load Simulation

1. Load regulation

 


9 October 2024

Transient Load Simulation

1. Load regulation

2. Overshoot

 


9 October 2024

Transient Load Simulation

1. Load regulation

2. Overshoot


3. Undershoot

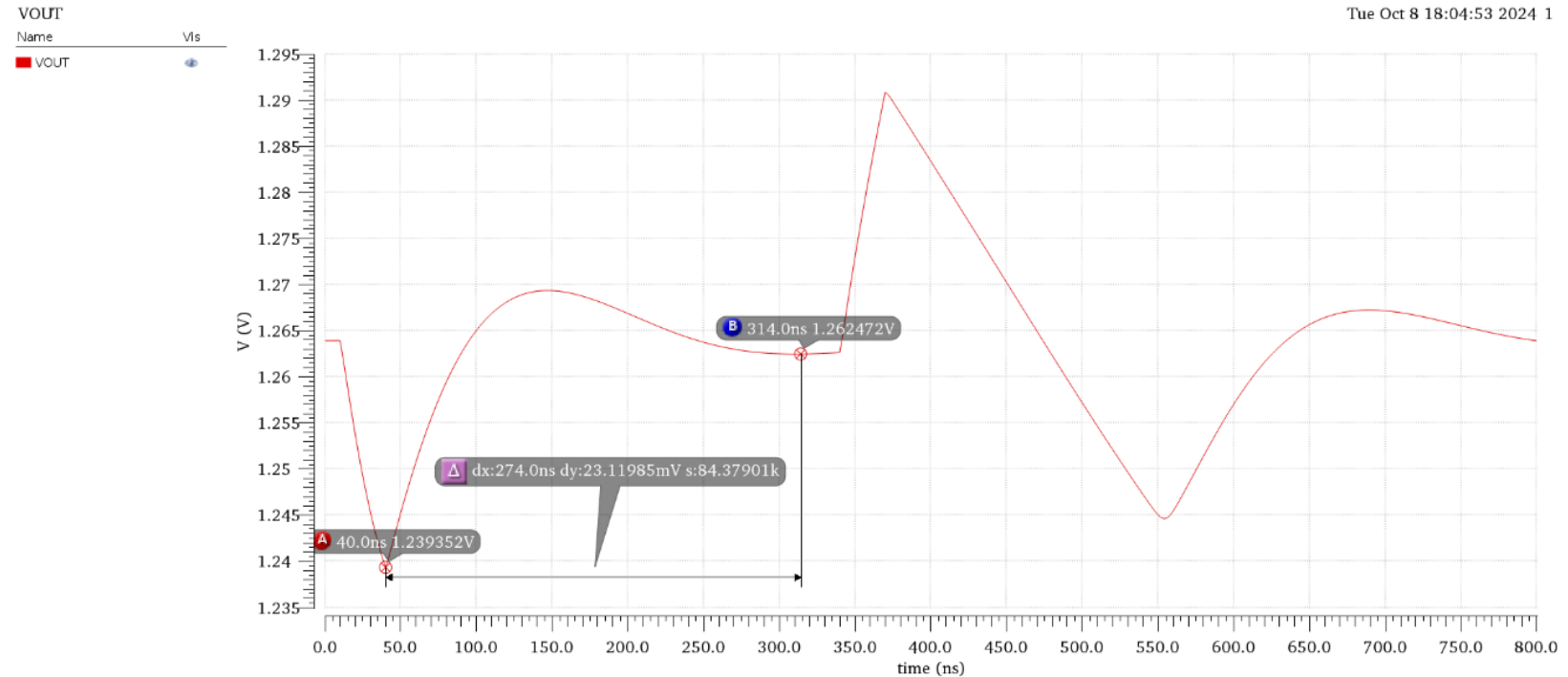

9 October 2024

Transient Input Simulation

1. Line regulation

 


9 October 2024

Stability Analysis and PSR

1. Phase Margin

loop gain phase

■ loop gain in dB
■ loop gain phase

 


9 October 2024

Stability Analysis and PSR

1. Phase Margin

2. PSR

 

9 October 2024

Figure of Merit

$$FOM = \frac{C_L * \Delta V_{out} * I_Q}{I_{L,max}^2} = 2.16 * 10^{-6} (ns)$$

Achieved Specs

Spec	Required	Achieved
Technology used	45nm CMOS	
Supply Voltage	2.4 V \rightarrow 3.5 V	—
Output Voltage	0.85 V \rightarrow 1.25 V	—
Untrimmed output voltage accuracy	$< \pm 6\%$	1%
Load Current	0.1 mA \rightarrow 150 mA	—
Undershoot/Overshoot	< 50 mV	27 mV
Phase margin	$> 45^\circ$	49°
Max Load Capacitance	1 nF	—
Line Regulation	< 2 mV/V	1.7 mV/V
Load Regulation	< 50 mV/A	9 mV/A
Power Supply Rejection at 1 MHz	30 dB	10 dB
Power Supply Rejection at 10 MHz	20 dB	4 dB
FOM	—	$2.16 * 10^{-6}$ (ns)

9 October 2024

Design Challenges



1. Why Al-shyoukh?

Fast-transient response and stability

2. PSR

Bypass device length, low-pass filter and El-Nozahy's paper

3. Line regulation

Magical mismatch effect

4. Load regulation

Decrease the bypass current normalized change

Thank You



For more details



Presented by

Mohamed Essam

Bilal Ramadan

Abdelrahman Abohendy

Mahmoud Saker

9 October 2024